

CD4017 Test 1 : LED Sequence Cycle

Goal: Using the CD4017 sequence 5 LED's to cycle through

Hypothesis: This should be simple. We just need to make sure to use Reset

Process:

1. Connect Q0 → Q4 to grounded LEDs with a resistor
2. Connect Reset to Q5 and Inhibit to GND
3. Connect Vcc and Ground
4. Connect an oscillating signal to Clock
 - this can be from the NE555 or through the arduino board

Conclusion:

- Works exactly how I thought it would
- Be careful connecting Q0-Q4 as the pins are not in order