

NESSS Test 1: Turn on an LED

Hypothesis: By connecting the power, ground, and reset I can turn on a LED by connecting it to the output

Process:

1. Use Arduino 5V and GND pin as a power supply
2. Connect 5V to pin 8 and GND to pin 1.
3. Connect Reset pin to the power supply
4. Use a 220Ω resistor and connect LED to Output

Result:

- The LED turned on just as expected.
- It has a measured voltage of ≈ 1.88
- By disconnecting the power LED turns
- This surprised me, by disconnecting the ground it doesn't turn off
- This might be the current grounding somewhere unexpected